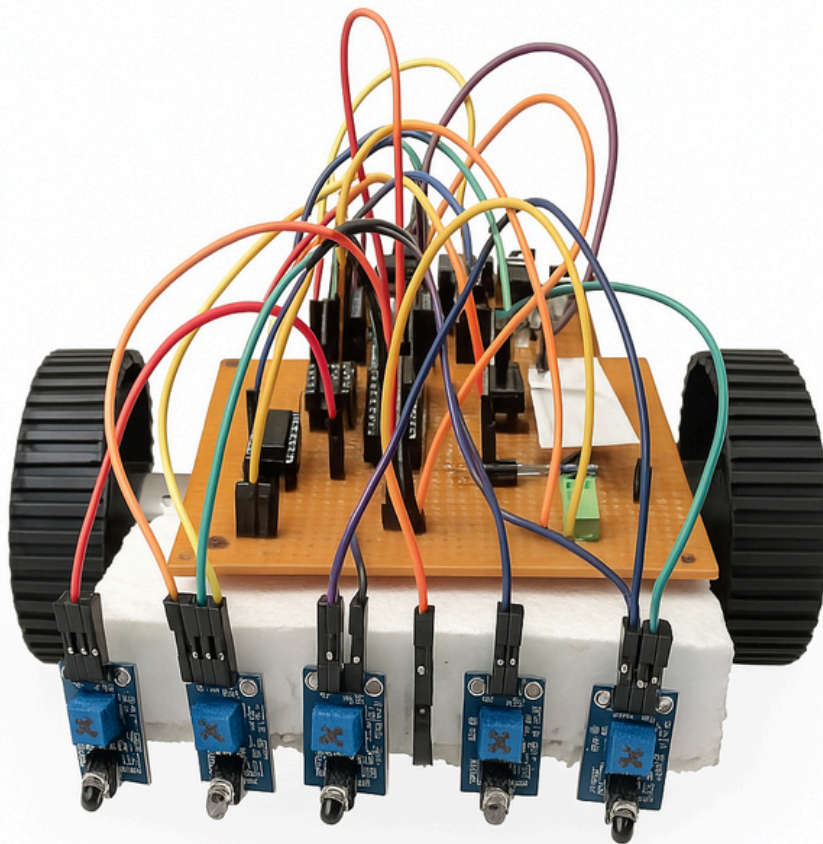




LINE FOLLOWER

•
•
•
•
TEAM Titanium Tech



8799165323|9586364504



drishti@svnit.ac.in

Drishti - A Revolutionary Concept

[drishti.svnit](https://www.facebook.com/drishti.svnit)



LINE FOLLOWER

Components Required

Sr. No	Components	Quantity(min)	Cost(approx.)(perpiece)
	Solderwire		
1	GCB(6"x4")	1roll	70
2	Screw	1	40
3	Connector	3	5
4	Maleandfemaleheader	2stripsofeach	20
5	Led (Red, Green, Blue)	6	4
6	Resistor (330ohm)	5	2
	Sliding Switch or Push		
7	button switch	1	20
8	IR Sensor	5	50
9	Arduino Uno board +Cable	1	550
10	LM7805Votageregulator	3	20
11	Lithium ion battery (11.1V)	1	350
12	BatterychargerforLi-Ion battery with connector	1	120
13	Jumperwire(femaletomale, female to female,male to male)	20+20+20	2
1	Singlestrand wire	1	3
4	L293D(motordriver)ICwith bed	1	0
16	Castorwheel (size 12Vmotor(200-300rpm)	1	25
17 5	Chassis	2	160 0
18	(readymade or self-made)	1	60
19	Wheels	2	30
20	Solder Iron	1	150
21	LClampformotor(incaseof self-made chassis)	2	15
	Diode(1N4007)		
22	Capacitor (1uFand 10uF)	2	2
23		2	3



8799165323|9586364504



drishti@svn timer.ac.in

Drishti - A Revolutionary Concept

drishti.svn timer



LINE FOLLOWER

Tech Specifications of Arduino UNO R3

Board	Name	Arduino UNO R3
	SKU	A000066
Microcontroller	ATmega328P	
USBconnector	USB-B	
	Built-inLEDPin	13
	DigitalI/O Pins	14
Pins	Analoginput pins	6
	PWMPins	6
	UART	Yes
	I2C	Yes
Communication	SPI	Yes
	I/OVoltage	5V
	Input voltage (Nominal)	7-12V
	DCCurrent per I/OPin	20 mA
	PowerSupply	
Power	Connector	Barrel Plug
	MainProcessor	ATmega328P 16 MHz
	USB-SerialProcessor	ATmega16U2 16 MHz 2KB
Clock speed	ATmega328P	SRAM, 32KB FLASH, 1KB EEPROM
Memory	Weight	25 g
	Width	53.4 mm
Dimension	Length	68.6 mm



8799165323|9586364504



drishti@svnit.ac.in


Drishti - A Revolutionary Concept

[drishti.svnit](https://www.facebook.com/drishti.svnit)

LINE FOLLOWER

Hardware Implementation

• Voltage Regulator

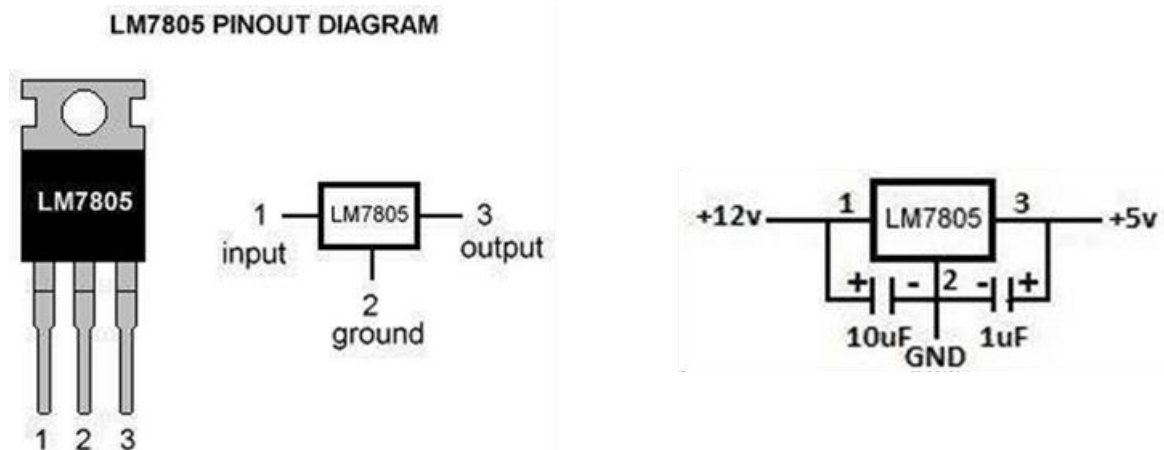

All 78xx IC are used to convert higher voltages to lower voltage of value "xx" as name of IC. Where, xx will be from 05 to 12. Input voltage should be from 7V to 35V. You will be using 7805 IC as you need 5V supply for microcontroller and other ICs. This IC is used to get regulated voltage supply of 5V. It is used in a circuit to convert 12V power supply to 5V. PIN1 will be connected to 12v or 9v input, PIN2 will be connected to GND. We will get regulated 5V output on PIN3. Capacitors can be connected between Input and GND and between Output and GND to filter out the AC component if any. Values of these capacitors should be in ratio 1:10 where lower valued capacitor will be connected between output and ground and the one with higher value will be connected between input and ground as shown.



8799165323|9586364504



drishti@svn timer.ac.in


Drishti - A Revolutionary Concept 

[@drishti.svn timer](https://www.facebook.com/drishti.svn timer) 

LINE FOLLOWER

♦ IR SENSOR

A line sensor is an Infra-Red or IR sensor which consists of an IR emitter and an IR receiver. The emitter is simply IR led and the detector is simply photodiode. Resistances and output voltages change in proportion to the magnitude of IR light received. The IR reflected back from the surface is received by the IR receiver if surface is light in colour. If transmitted IR signal is received back, this sensor gives a 5v (logic 1) output or 0v (logic 0) output depending on IR circuitry and vice versa for no detection.

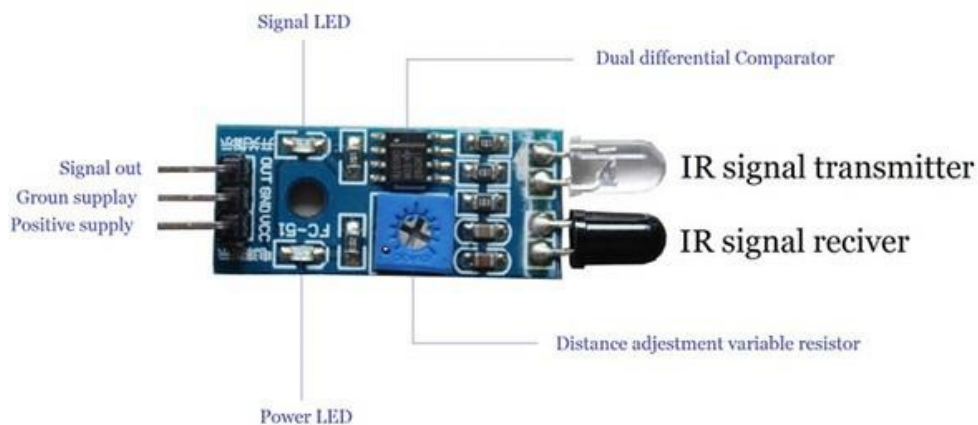

- 5V or VCC pin should be given 5V input to switch the sensor on.
- Ground should be connected to ground.
- OUT pin will give logic 1 or 0 depending on IR when it detects a surface bright in color.
- Component shaped "plus" in above diagram is a potentiometer which is used to calibrate IR sensor according to right conditions of surroundings.

This sensor will act as input for our Microcontroller to detect whether we are on white line or somewhat deviated.



8799165323|9586364504




drishti@svn timer.ac.in

Drishti - A Revolutionary Concept 

[drishti.svn timer](https://www.facebook.com/drishti.svn timer) 

LINE FOLLOWER

♦ Motor Driver (L293D)

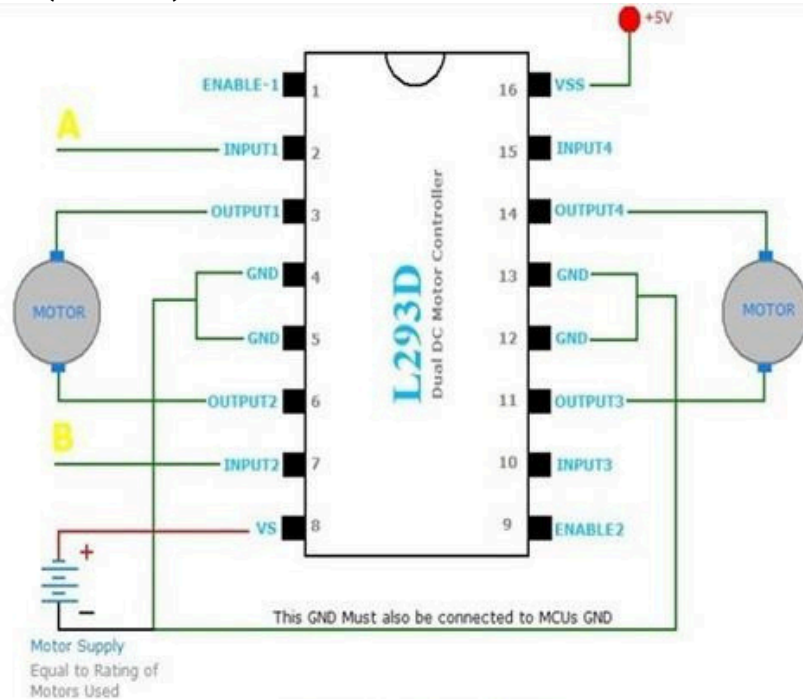

Motor Controller Using L293D

- Motor driver is the IC used to control motor.
- Enable 1, 2 and Enable 3, 4 are used to activate corresponding sides.
- Input 1, 2, 3 and 4 are used to give direction signals to L293D.
- Output 1, 2, 3 and 4 are used to connect motors to L293D.
- Vcc1 is given 5V signal w.r.t GND to the IC L293D to activate it.
- Vcc2 is given 12V supply w.r.t GND to run motors.
- All 4 GND pins are reconnected to the common ground of circuit.
- Voltage output from microcontroller will go to input pins of L293D.
- Enable 1 (PIN1) and Enable 2 (PIN9) will be connected to 5V to activate the motor driver circuit.
- Vs (12Volts) (PIN8) will be provided to drive motor. Vss (PIN16) is connected to 5V required to switch on IC.



8799165323 | 9586364504



drishti@svn timer.ac.in

Drish ti - A Revolutionary Concept 

[@drishti.svn timer](https://www.facebook.com/drishti.svn timer) 



LINE FOLLOWER

- **Capacitor**

Capacitors (originally called electrical condensers) are analog electrical components that can collect and store electrical energy. As a direct current flows into a capacitor, it charges with energy and releases an alternating current flow back into the circuit.

- **Diode**


1N4007 belongs to the silicon family of 1N400X series. It is a general-purpose rectifying diode that serves its purpose of converting alternating current signals (AC) to direct current signals (DC) in electronic products.

- **Interfacing Arduino With The Computer**

You need to install the Arduino IDE (Version 1.8.19) from the given link below

Download Link :- <https://www.arduino.cc/en/software>

Complete Schematic of Line Follower

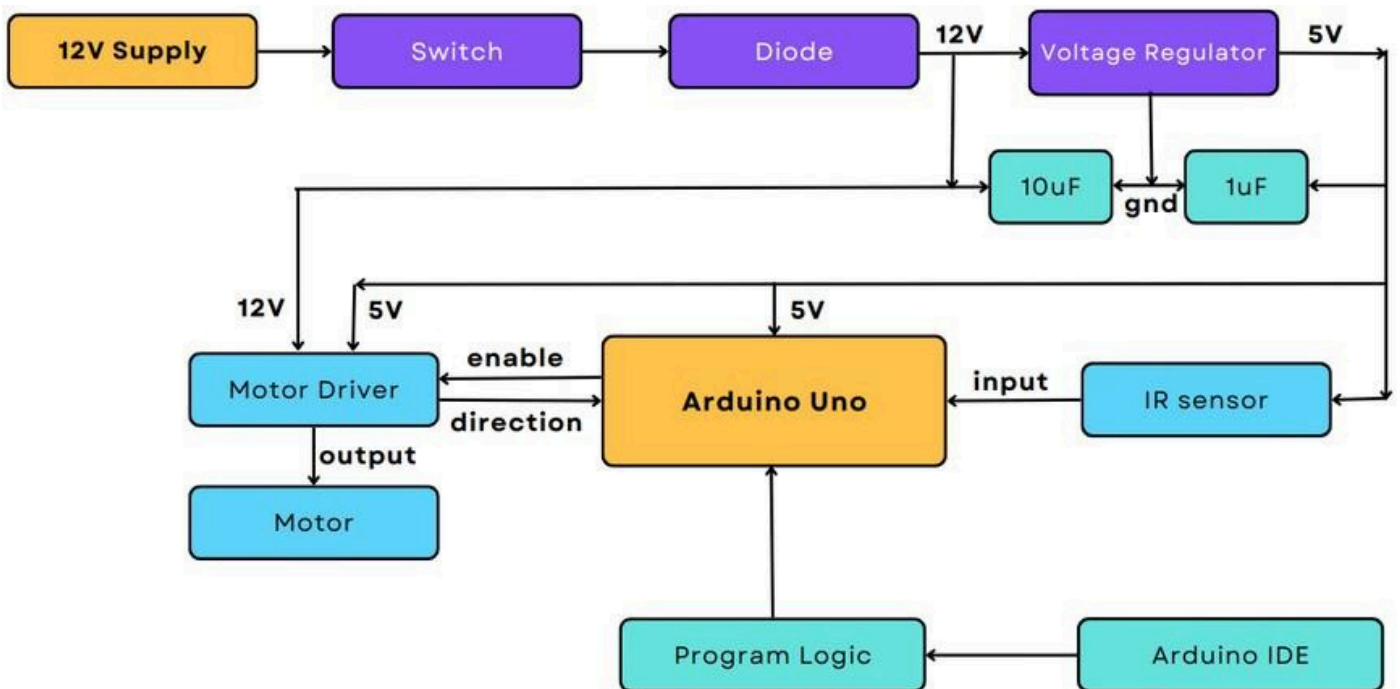

8799165323|9586364504



drishti@svn timer.ac.in

Drishti - A Revolutionary Concept

[drishti.svn timer.ac.in](https://www.drishti.svn timer.ac.in)



LINE FOLLOWER

♦ Reference Link

These are some reference links for the programming of Arduino board.

- ♦ <https://docs.arduino.cc/tutorials/uno-rev3/Blink>
- ♦ <https://docs.arduino.cc/tutorials/uno-rev3/AnalogReadSerial>
- ♦ <https://docs.arduino.cc/tutorials/uno-rev3/DigitalReadSerial>

Note: For safety purpose buy Capacitors (1uF and 10uF)

Miscellaneous Items:

1. Digital Multimeter
2. Double sided tape
3. Stripper
4. Insulation Tape
5. Screw Driver (small)

♦ Precautions

- ♦ DONOT solder any microcontroller or IC directly on the GCB, always use an IC bed or make one with female headers.
- ♦ DONOT short positive and negative terminals of supply with each other.
- ♦ NEVER SUPPLY VOLTAGE WITH REVERSE POLARITY TO YOUR CIRCUIT, it will cost you a lot.
- ♦ Make sure your microcontroller and other ICs get 5V from 7805 circuit wherever needed. DONOT GIVE 12V TO ANY COMPONENT UNLESS IT IS MENTIONED.
- ♦ Use diodes on 12V supply on positive terminal as reverse polarity protection
- ♦ Add an insulation below your circuit board to avoid shorting.
- ♦ Always mark polarities on connectors. Ideal convention is Left side positive and Right side negative.
- ♦ IR sensors detect infrared radiation so they will NOT work as expected in sunlight.
- ♦ Make common ground for all ICs present on your GCB.
- ♦ Always check the orientation of your ICs before placing them in their beds.
- ♦ Try to minimize jumps when you design your circuit.



8799165323|9586364504



drishti@svn timer.ac.in